

Analytical Calculation

We are going to use 3 phase diode rectifier and buck converter

3 Φ Diode Rectifier

$$V_{dc} = \frac{3\sqrt{2}}{\pi} V_{\ell\ell} - \frac{3}{\pi} \omega L_s I_d$$

Min

$$V_{\ell\ell} = 15 V_{\ell\ell}$$

$$V_{dc} = \frac{3\sqrt{2} \times 15}{\pi} - \frac{3}{\pi} \omega L_s I_d$$

Assume no commutation

$$V_{dc} = 20.25 V$$

Max

$$V_{\ell\ell} = 25 V_{\ell\ell}$$

$$\frac{3\sqrt{2} \times 25}{\pi} - \frac{3}{\pi} \omega L_s I_d$$

With Commutation

$$V_{dc} = 33.76$$

Buck Converter

$$V_o = 12V$$

$$V_o = D V_d$$

$$I_{L_{peak}} = \frac{1}{L} (V_d - V_o) D T_s$$

$$L_{min} = \frac{R(1-D)}{2f_s}$$

$$V_{DC} = 24 \rightarrow D_{max} = 0.35$$

$$I_{L_{peak}} = \frac{1}{L} (22) \cdot 0.35 \cdot T_s$$

$$L_{min} = R \frac{0.65 \times T_s}{2}$$

$$I_{L_{peak}} \times L = \frac{7.7}{f_s}$$

If I want to use $L = 220 \mu H$
with $\%20$ tolerance

$$L_{min} = 200 \mu H$$

$$L_{min} = \frac{R \cdot 0.325}{f_s}$$

$$I_{L_{peak}} \times f_s = 35000$$

$$\text{if } f_s = 70 \text{ kHz}$$

$$I_{L_{peak}} = 2A$$

$220 \mu H / 2A$
inductor exist in

discreet but I need to put safety margin

SRI1204 $\%20$ tolerance

$$f_s = 50 \text{ kHz} \rightarrow I_{L_{peak}} = 0.7A$$

Exist and lots of options

$$f_s = 80 \text{ kHz} \rightarrow I_{L_{peak}} = 0.44A$$

to small current
all inductors have higher
current capability

So \rightarrow

$$\begin{array}{l} f_s = 50 \text{ kHz} \\ L = 220 \mu\text{H} \end{array}$$

$$> I_{L\text{peak}} = 0.7 \text{ A}$$

$$L_{\min} = 200 \mu\text{H}$$

$$L_{\min} = R \cdot \frac{0.325}{f_s}$$

$$R = 30.76 \Omega$$

Check Does this values valid for small V_{DC} :

$$V_{DC} = 20 \rightarrow D_{\max} = 0.6$$

$$I_{L\text{peak}} = \frac{1}{L} \cdot 8 \cdot 0.35 \cdot T_s$$

$$L_{\min} = \frac{R \cdot 0.4 \cdot T_s}{2}$$

$$I_{L\text{peak}} = \frac{1}{220 \mu\text{H}} \times 8 \times 0.35 \times \frac{1}{50 \text{ kHz}} = 0.25 \text{ A} \checkmark$$

$$L_{\min} = \frac{31 \times 0.4}{2 \times 50 \text{ kHz}}$$

$$R \geq 45 \Omega$$

We need to change R . For putting safety margin

Let's make $R = 100 \Omega$

$$\frac{\Delta V_o}{V_o} = \frac{(1-D) T_s^2}{32 \pi^2 f_c^2}$$

$$\odot \quad < \frac{\Delta V_o}{V_o} < \frac{(T_s)^2}{8LC}$$

$$\frac{(T_s)^2}{8 \times 220 \times 10^{-6} \times C} = \frac{2.2727 \times 10^7}{C}$$

We need to find a capacitor that has small ESR and choose C as big as possible

MOSFET

Maximum voltage in the circuit = 34V. Our mosfet has at least 45V voltage rating.

