



$R_{bat}$  : Typically between  $0.1\Omega$  and  $0.9\Omega$ , take it as  $0.5\Omega$

$$V_{bat\max} = 12V$$

$$V_{in} \approx 33V \quad (\text{ideal and max case})$$

If  $R_{bat} = 0.5\Omega$  and battery is fully charged,  $V_o$  must be  $17V$  to supply  $10A$  ( $V_{bat} \approx 4V$ )

If  $R_{bat} = 0.5\Omega$  and battery is close to dead,  $V_o$  must be  $9V$

$$D = \frac{V_{out}}{V_{in} \times \eta} \rightarrow D_{\text{case-1}} = \frac{17}{33 \times 0.9} = 0.572$$

↓  
efficiency  
of the conv.  
typ. 0.9

$$D_{\text{case-2}} = \frac{9}{33 \times 0.9} = 0.3$$

Rough est. of  $D$  :  $0.3 \leq D \leq 0.575$

$$\Delta I_L = \frac{(V_{IN(max)} - V_{out}) \times \Delta}{f_s \times L} \rightarrow L = \frac{V_{out} \times (V_{IN} - V_{out})}{\Delta I_L \times f_s \times V_{IN}}$$

\* (Selection Criteria)  $\rightarrow I_{sw(max)} = \frac{\Delta I_L}{2} + I_{out(max)} \rightarrow \approx 12-13 \text{ A}$  for us

$\downarrow$   
 MOSFET current  
 for us

$$L = \frac{17 \times (33 - 17)}{2 \times 50e3 \times 33} = 82.4 \mu\text{H} \rightarrow \text{case 1}$$

$$L = \frac{9 \times (33 - 9)}{2 \times 50e3 \times 33} = 65.45 \mu\text{H} \rightarrow \text{case 2}$$

$L$  must be,  $L > 82.4 \mu\text{H}$  //

Diode: use schottky diodes!

$$I_f = I_{out(max)} \times (1 - D)$$

$\downarrow$   
 $\approx 12 \text{ A}$

$\hookrightarrow \text{min} = 0.3$

$$I_F = 12 \times (1 - 0.3) = 8.4 \text{ A}$$

Count:

$$C_{out(min)} = \frac{\Delta I_L}{8 \times f_s \times \Delta V_{out}}$$

$$\Delta V_{out} = ESR \times \Delta I_L$$

$$C_{out(min)} = \frac{2}{8 \times 50e3 \times 2} = 2.5 \mu F$$

→ Simülasyonda Denedim Sonuçlar Mantıklı  
Çıkmadı

$$V_o = D V_{in}$$

$$I_{Lmin} = V_o \left[ \frac{1}{R} - \frac{(1-D)}{2Lf} \right] \rightarrow L = \frac{(1-D)RV_o}{2f(V_o - RI_{Lmin})}$$

$$I_{Lmax} = V_o \left[ \frac{1}{R} + \frac{(1-D)}{2Lf} \right] \rightarrow L = \frac{RV_o(1-D)}{2f(RI_{Lmax} - V_o)}$$

$$L_{min} = \frac{(1-D_{max})R_{max}}{2f}$$

$$L_{min} = V_o \frac{(1-D)}{\Delta i_L f}$$

$$C_{in} = \frac{(1-D) \cdot D \cdot I_{omax}}{f \Delta V_{in}}$$

$$C_o = \frac{(1-D_{min})}{8Lf^2 \left( \frac{\Delta V_o}{V_o} \right)}$$

$$V_{out} = 14V$$

$$V_{in} = 33V$$

$$D = 0.424$$

$$L_{min} = 14 \frac{(1 - 0.424)}{2 \times 50e3} = 80.64 \mu H$$

$$L_{I_{Lmin}} = \frac{(1 - 0.424) \times 0.5 \times 14}{2 \times 50 \times 10^3 \times (14 - 0.5 \times 9)} = 4.24 \mu H$$

$$L_{I_{Lmax}} = \frac{(1 - 0.424) \times 0.5 \times 14}{2 \times 50 \times 10^3 \times (0.5 \times (1 - 14))} =$$

3

?

0

$$L > 80.64 \mu H$$

$$C_{in} = \frac{(1 - 0.5) \times 0.5 \times 11}{50e3 \times 8} = 6.875 \mu F$$

$$C_o = \frac{(1 - 0.3)}{8 \times 200e-6 \times (50e3)^2 \left( \frac{4}{12} \right)} = 525 nF$$